

# **Computer Organization and Architecture Laboratory**

## **Assignment 3**


**Group 22**

Nikhil Saraswat(20CS10039)

Amit Kumar (20CS30003)

## PART 2: Carry Look-ahead Adders

### 1. 4-bit carry look-ahead adder

 

The carry lookahead adder reduces the delay in calculating the sum by calculating the carries concurrently rather than waiting for the carry from the previous block to ripple, as is the case with the ripple carry adder.

The carry look-ahead adder's logic is as follows:

For  $-1 < i < 4$  ,

$G[i] = in1[i] \& in2[i]$

$P[i] = in1[i] \wedge in2[i]$

Take  $c_{in}$  to be  $carry[0]$  then:

For  $-1 < i < 4$  ,

$sum[i] = P[i] \wedge carry[i]$

$carry[i] = G[i-1] \vee (P[i-1] \& carry[i-1])$

After Recursively expanding :

$$\text{carry}[1] = G[0] \mid (P[0] \ \& \ \text{carry}[0]) = G[0] \mid (P[0] \ \& \ c\_in)$$
$$\text{carry}[2] = G[1] \mid (P[1] \ \& \ \text{carry}[1]) = G[1] \mid (P[1] \ \& \ G[0]) \mid (P[1] \ \& \ P[0] \ \& \ c\_in)$$
$$\text{carry}[3] = G[2] \mid (P[2] \ \& \ \text{carry}[2]) = G[2] \mid (P[2] \ \& \ G[1]) \mid (P[2] \ \& \ P[1] \ \& \ G[0]) \mid (P[2] \ \& \ P[1] \ \& \ P[0] \ \& \ c\_in)$$
$$\text{carry}[4] = G[3] \mid (P[3] \ \& \ \text{carry}[3]) = G[3] \mid (P[3] \ \& \ G[2]) \mid (P[3] \ \& \ P[2] \ \& \ G[1]) \mid (P[3] \ \& \ P[2] \ \& \ P[1] \ \& \ G[0]) \mid (P[3] \ \& \ P[2] \ \& \ P[1] \ \& \ P[0] \ \& \ c\_in)$$

## 2. 4-bit carry look-ahead adder (augmented)


Instead of generating the carry out, we give the block propagate and generate as output, which is then used by the carry lookahead unit.

This results in a modular design that allows us to create 16, 32, and 64 bit adders by combining the block propagate and generate from lower levels rather than rippling the carry out every time.

The other logic is the same as in a standard 4-bit CLA.

The propagation and generation of blocks are calculated as follows:

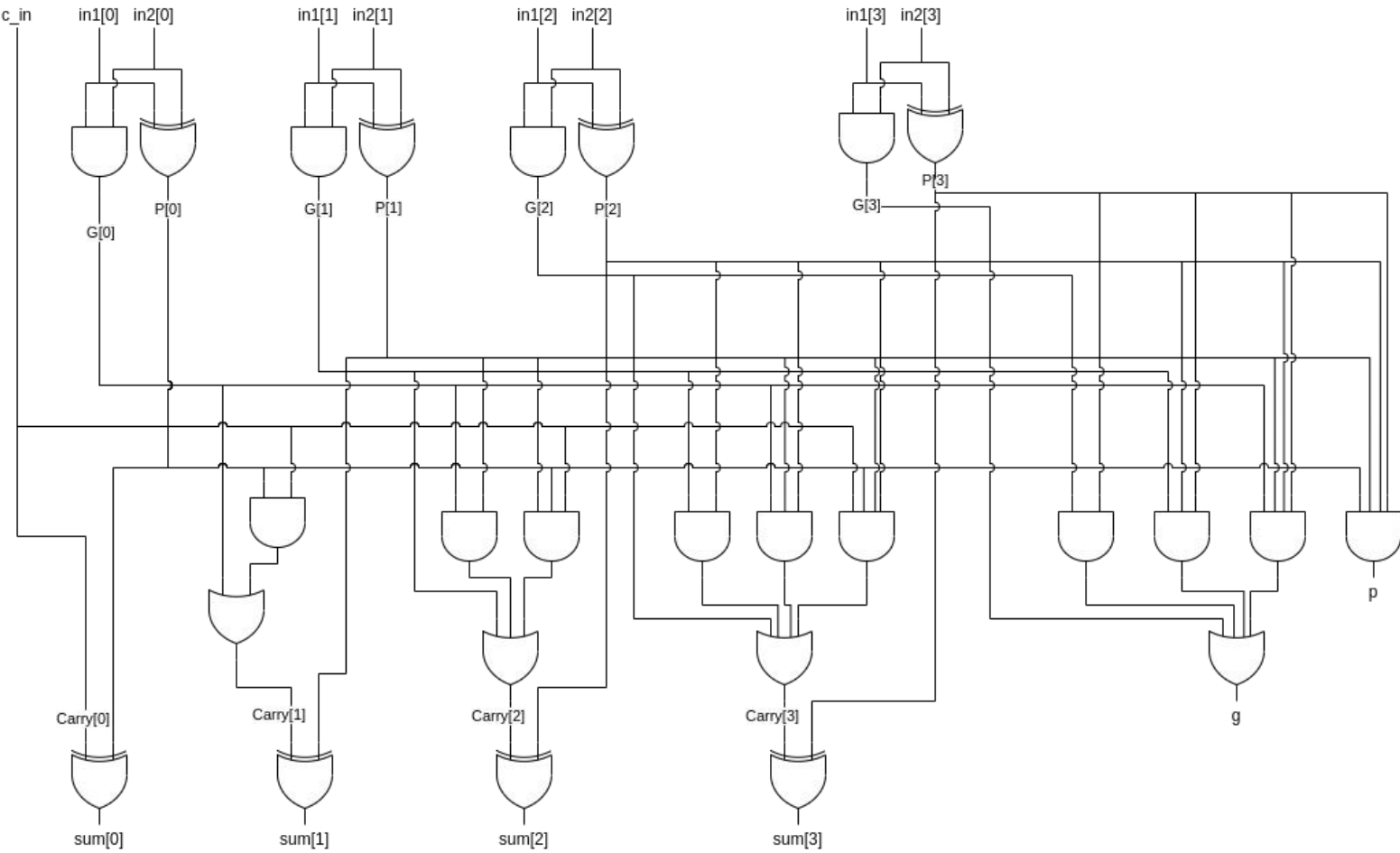
$$p = P[3] \ \& \ P[2] \ \& \ P[1] \ \& \ P[0]$$
$$g = G[3] \mid (P[3] \ \& \ G[2]) \mid (P[3] \ \& \ P[2] \ \& \ G[1]) \mid (P[3] \ \& \ P[2] \ \& \ P[1] \ \& \ G[0])$$


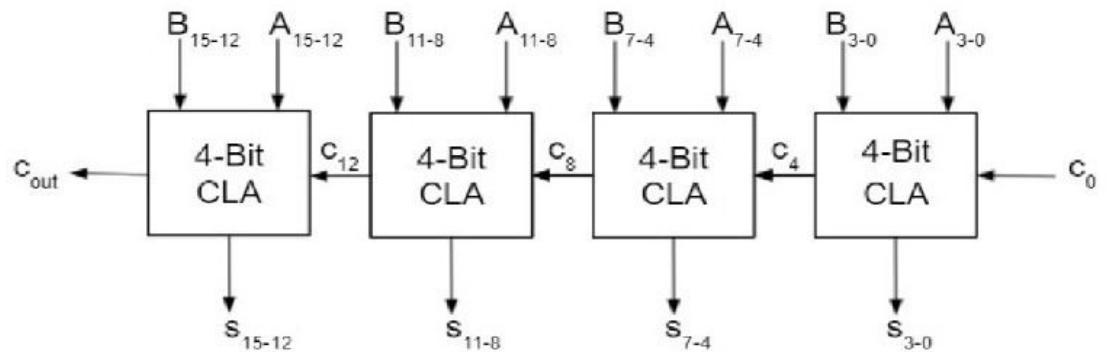
### 3. 16-bit carry look-ahead adder (ripple carry out)

This 16-bit adder is constructed by cascading four 4-bit CLAs and rippling the carry out from one block to the next, as illustrated in the figure.

Here, carry[2:0] are internal carries being rippled from one block to another.



### 4. 16-bit carry look-ahead adder (look-ahead carry unit)

Let  $P[3:0]$  and  $G[3:0]$  represent the block propagate and generate of the four 4-bit CLAs, respectively.

Instead of rippling the carry out from one block to the next, we can reduce the delay in the circuit by adding an additional lookahead unit that calculates these carries simultaneously.

This eliminates the need for subsequent blocks to wait for the previous block's carry.

This also leads to a modular design in which we can calculate the block propagation and generation of the entire 16-bit CLA and use it later for higher order adders.

The logic for the lookahead carry unit is as follows:

Take  $c_{in}$  to be  $carry[0]$  then

$carry[i] = G[i-1] \mid (P[i-1] \& carry[i-1]), 1 \leq i \leq 4$

After Recursively expanding

$$\text{carry}[1] = G[0] \mid (P[0] \ \& \ \text{carry}[0]) = G[0] \mid (P[0] \ \& \ c\_in)$$

$$\text{carry}[2] = G[1] \mid (P[1] \ \& \ \text{carry}[1]) = G[1] \mid (P[1] \ \& \ G[0]) \mid (P[1] \ \& \ P[0] \ \& \ c\_in)$$


$$\text{carry}[3] = G[2] \mid (P[2] \ \& \ \text{carry}[2]) = G[2] \mid (P[2] \ \& \ G[1]) \mid (P[2] \ \& \ P[1] \ \& \ G[0]) \mid (P[2] \ \& \ P[1] \ \& \ P[0] \ \& \ c\_in)$$

$$\text{carry}[4] = G[3] \mid (P[3] \ \& \ \text{carry}[3]) = G[3] \mid (P[3] \ \& \ G[2]) \mid (P[3] \ \& \ P[2] \ \& \ G[1]) \mid (P[3] \ \& \ P[2] \ \& \ P[1] \ \& \ G[0]) \mid (P[3] \ \& \ P[2] \ \& \ P[1] \ \& \ P[0] \ \& \ c\_in)$$

Block propagate p and generate g are calculated as:

$$p = P[3] \ \& \ P[2] \ \& \ P[1] \ \& \ P[0]$$
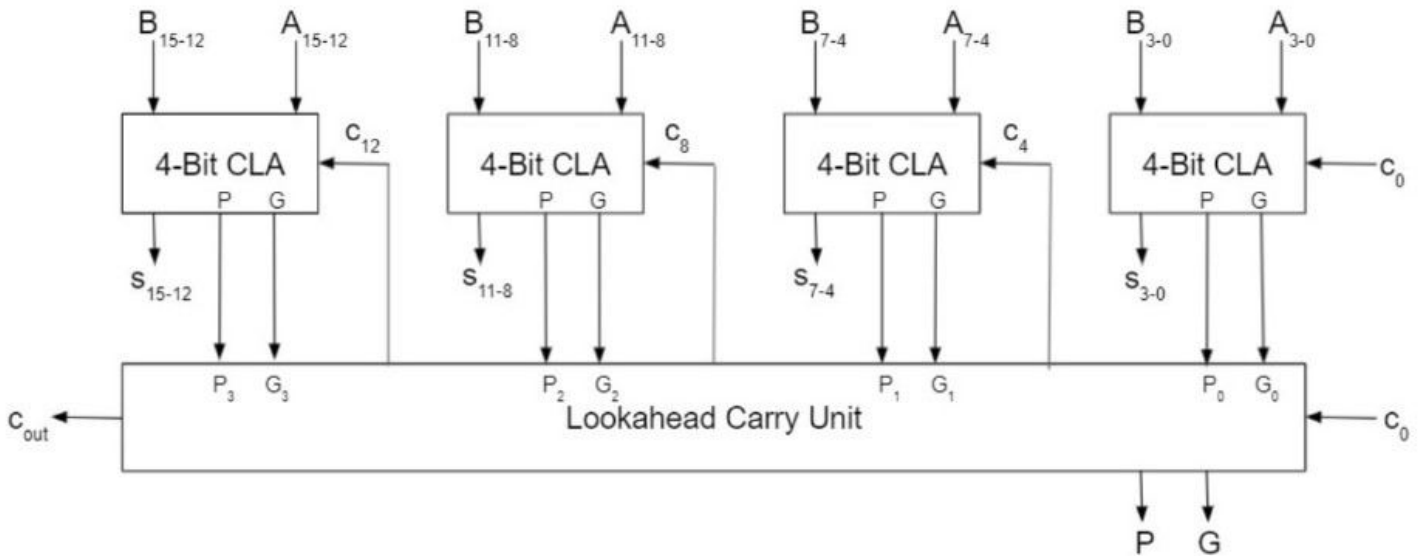
$$g = G[3] \mid (P[3] \ \& \ G[2]) \mid (P[3] \ \& \ P[2] \ \& \ G[1]) \mid (P[3] \ \& \ P[2] \ \& \ P[1] \ \& \ G[0])$$



## SYNTHESIS SUMMARY

	16-bit carry look-ahead adder (ripple carry out)	16-bit carry look-ahead adder (look-ahead carry unit)
Delay (in ns)	6.200	5.013
Number of Slice LUTs	25 out of 63400	44 out of 63400
Number of bonded IOBs	50 out of 210	52 out of 210
Levels of Logic	11	8

A CLA with an additional lookahead carry unit outperforms simply rippling the carry at the expense of more LUTs.

### - Comparison with 4-bit RCA

4-bit	Delay (in ns)	Number of Slice LUTs	Logic Levels
CLA	2.123	6 out of 63400	4
RCA	3.194	8 out of 63400	10

### - Comparison with 16-bit RCA

It is clear that a CLA is significantly faster than an RCA. In addition, the LUTs used are nearly half that of an RCA.


16-bit	Delay (in ns)	Number of Slice LUTs	Logic Levels
CLA	3.768	44 out of 63400	8
RCA	6.167	24 out of 63400	10

## Post Route Simulation Screenshots:

- wrapper


	Met	Constraint	Check	Worst Case Slack	Best Case Achievable	Timing Errors	Timing Score
1	Yes	<a href="#">Autotimespec constraint for clock net clk_BUFGP</a>	SETUP HOLD	0.202ns	3.768ns	0	0

• RCA\_4bit

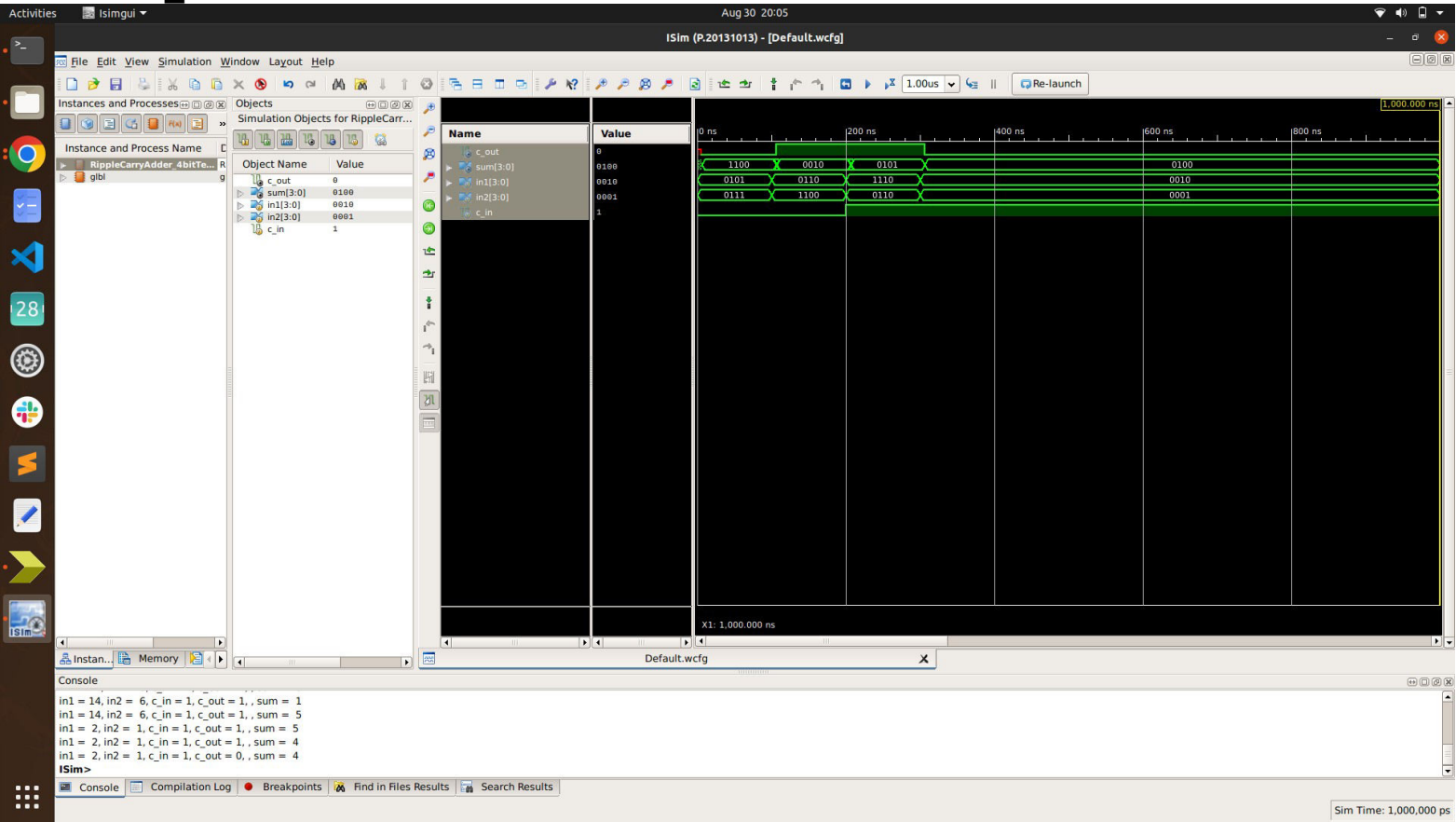


• CLA\_16bit\_with LCU



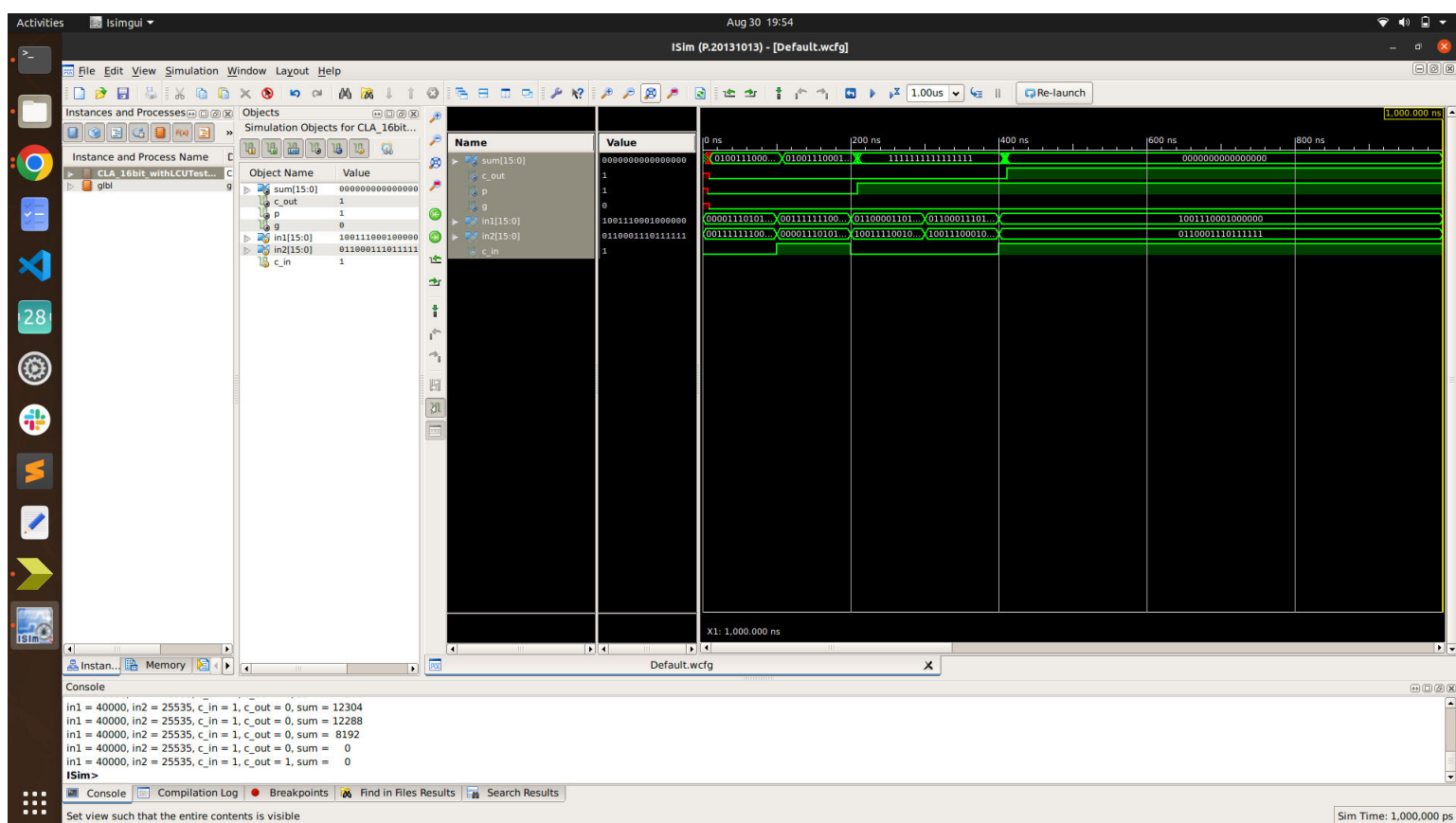

- LCA\_16bit\_ripple

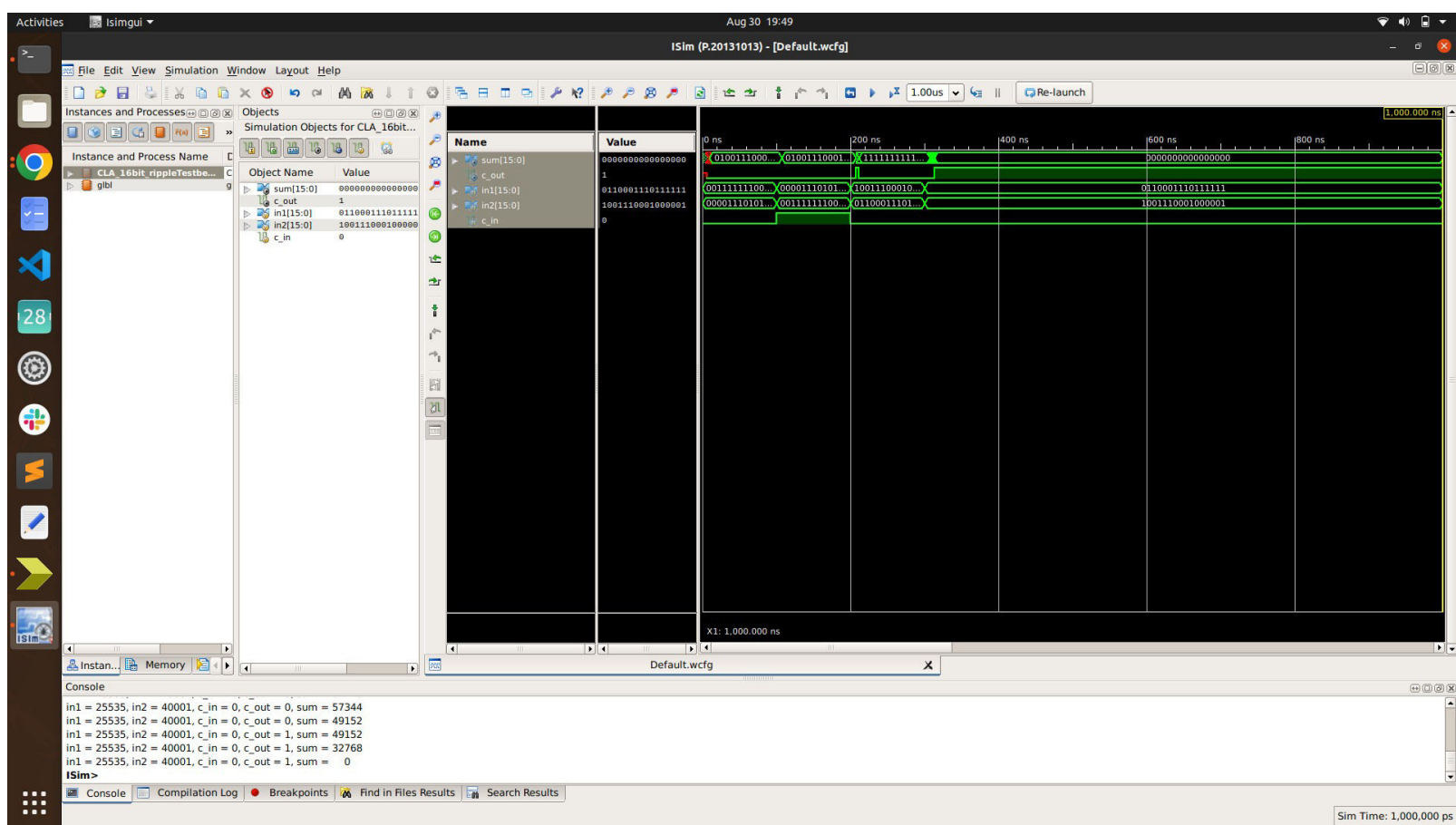

- 4-bit-CLA

Activities

Isimgui

Aug 30 19:43

ISim (P.20131013) - [Default.wcfg]

File Edit View Simulation Window Layout Help

Instances and Processes

Simulation Objects for CLA\_4bitT...

Instance and Process Name

CLA\_4bitTestbench

gibi

Object Name

Value

c\_out

0

sum(3:0)

0010

c\_in

1

in1[3:0]

0001

in2[3:0]

0000

Name

Value

c\_out

0

sum

0010

c\_in

1

in1

0001

in2

0000

0 ns

100 ns

200 ns

300 ns

400 ns

500 ns

600 ns

700 ns

800 ns

900 ns

1,000.000 ns

1000

0000

0110

0010

0100

0011

0101

0001

0100

1100

0010

0000

X1: 1,000.000 ns

Default.wcfg

Console

in1 = 3, in2 = 2, c\_in = 1, c\_out = 0, sum = 2

in1 = 3, in2 = 2, c\_in = 1, c\_out = 0, sum = 6

in1 = 5, in2 = 0, c\_in = 1, c\_out = 0, sum = 6

in1 = 1, in2 = 0, c\_in = 1, c\_out = 0, sum = 6

in1 = 1, in2 = 0, c\_in = 1, c\_out = 0, sum = 2

ISim>

Console

Compilation Log

Breakpoints

Find in Files Results

Search Results

Sim Time: 1,000,000 ps