

Computer Organization and Architecture Laboratory

Assignment 3

Group 22


Nikhil Saraswat (20CS10039)

Amit Kumar (20CS30003)

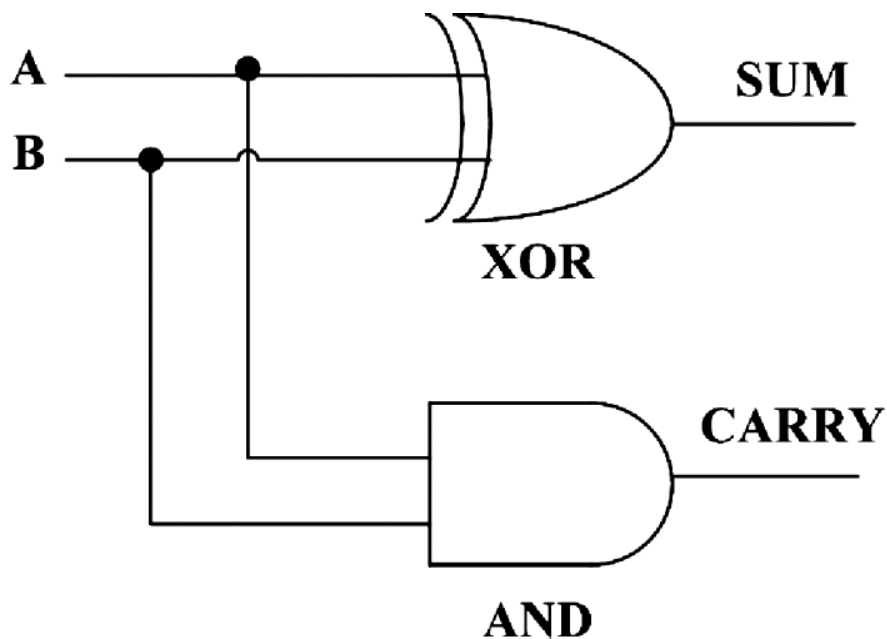PART 1: RCA

Half adder

Half adder is the simplest of all adder circuits. Half adder is a combinational arithmetic circuit that adds two numbers and produces a sum bit (s) and carry bit (c) both as output. The addition of 2 bits is done using a combination circuit called a Half adder. The input variables are augend and addend bits and output variables are sum & carry bits. A and B are the two input bits.




Inputs		Outputs	
A	B	Sum	C_out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Boolean Logic:

```
c_out = a & b  
sum = a ^ b
```

Full adder

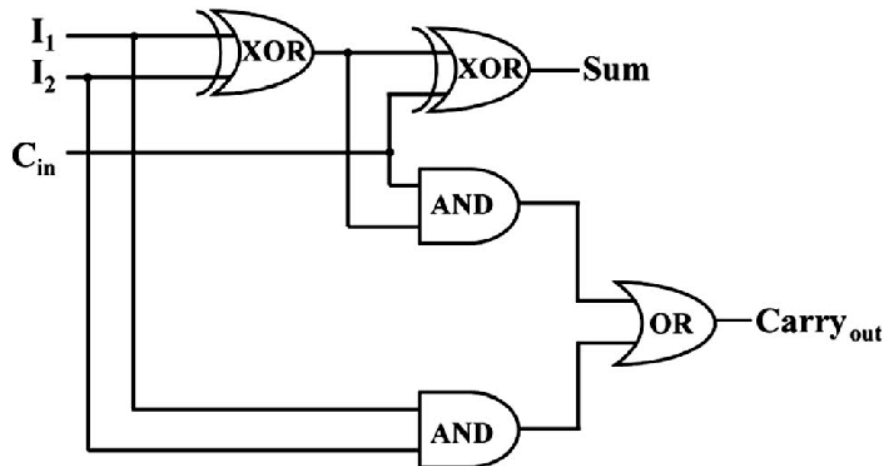A full adder circuit is central to most digital circuits that perform addition or subtraction. It is so called because it adds together two binary digits, plus a carry-in digit to produce a sum and carry-out digit. It therefore has three inputs and two outputs.



Inputs			Outputs	
I_1	I_2	C_{in}	Sum	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Boolean Logic:

$$\begin{aligned}\text{sum} &= a \wedge b \wedge c_{in} \\ c_{out} &= (a \& b) \mid (c \& (a \wedge b))\end{aligned}$$


RCA

A structure of multiple full adders is cascaded in a manner to give the results of the addition of an n bit binary sequence. This adder includes cascaded full adders in its structure so, the carry will be generated at every full adder stage in a ripple-carry adder circuit. These carry output at each full adder stage is forwarded to its next full adder and there applied as a carry input to it. This process continues up to its last full adder stage. So, each carry output bit is rippled to the next stage of a full adder. By this reason, it is named as "RIPPLE CARRY ADDER". The most important feature of it is to add the input bit sequences whether the sequence is 4 bit or 5 bit or any.


8-bit RCA

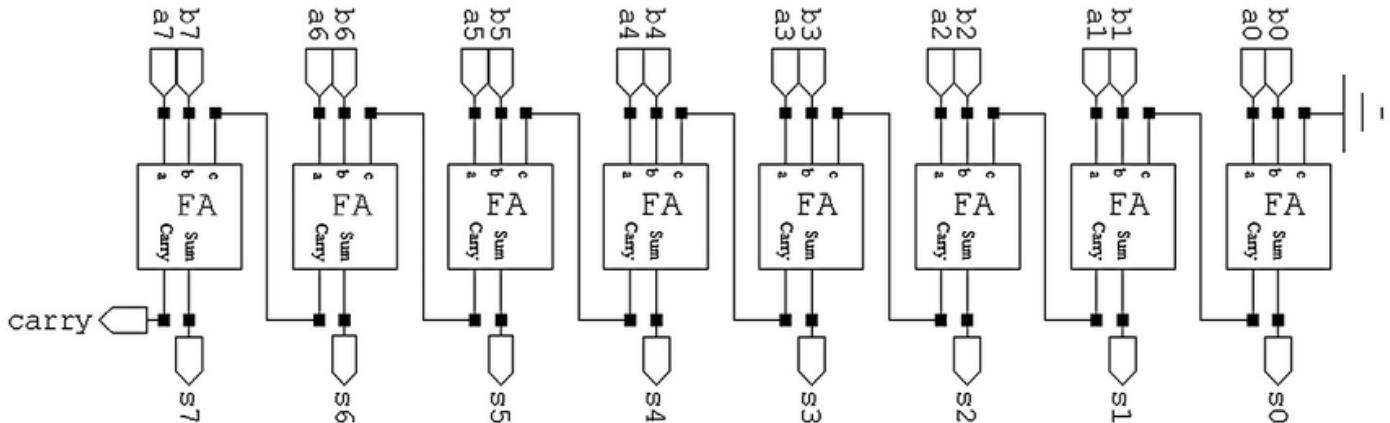


16-bit adder

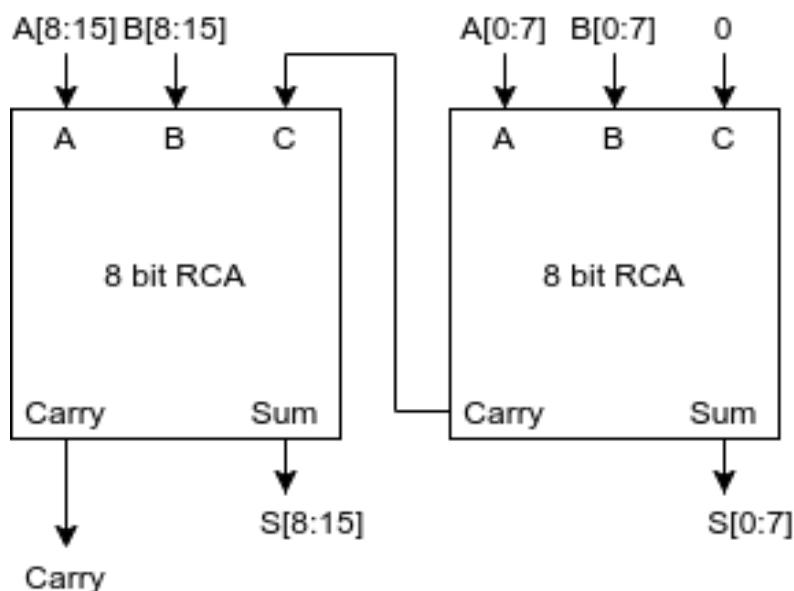

32-bit adder

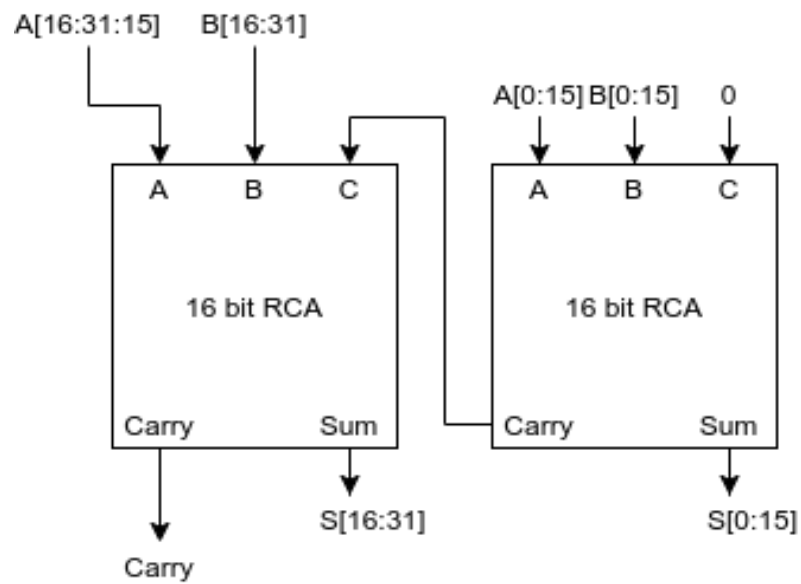

64-bit adder

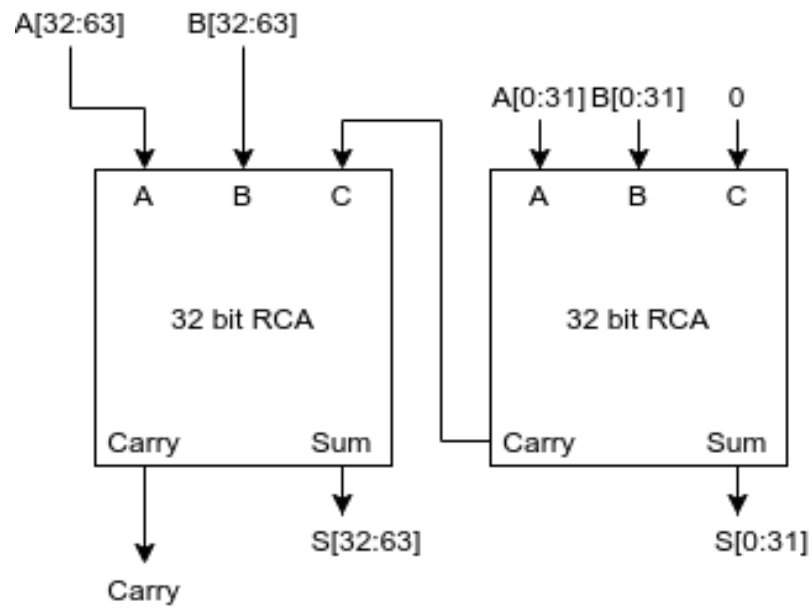


SYNTHESIS SUMMARY


Circuit	Delay (in ns)	Logic Levels	Number of Slice LUTs	Number of bonded IOBs
8-bit RCA	3.471	6	12 / 63400	26 / 210
16-bit RCA	6.167	10	24 / 63400	50 / 210
32-bit RCA	11.559	18	48 / 63400	98 / 210
64-bit RCA	22.343	34	96 / 63400	194 / 210

Post Route Simulation Screen Shots:


Half adder

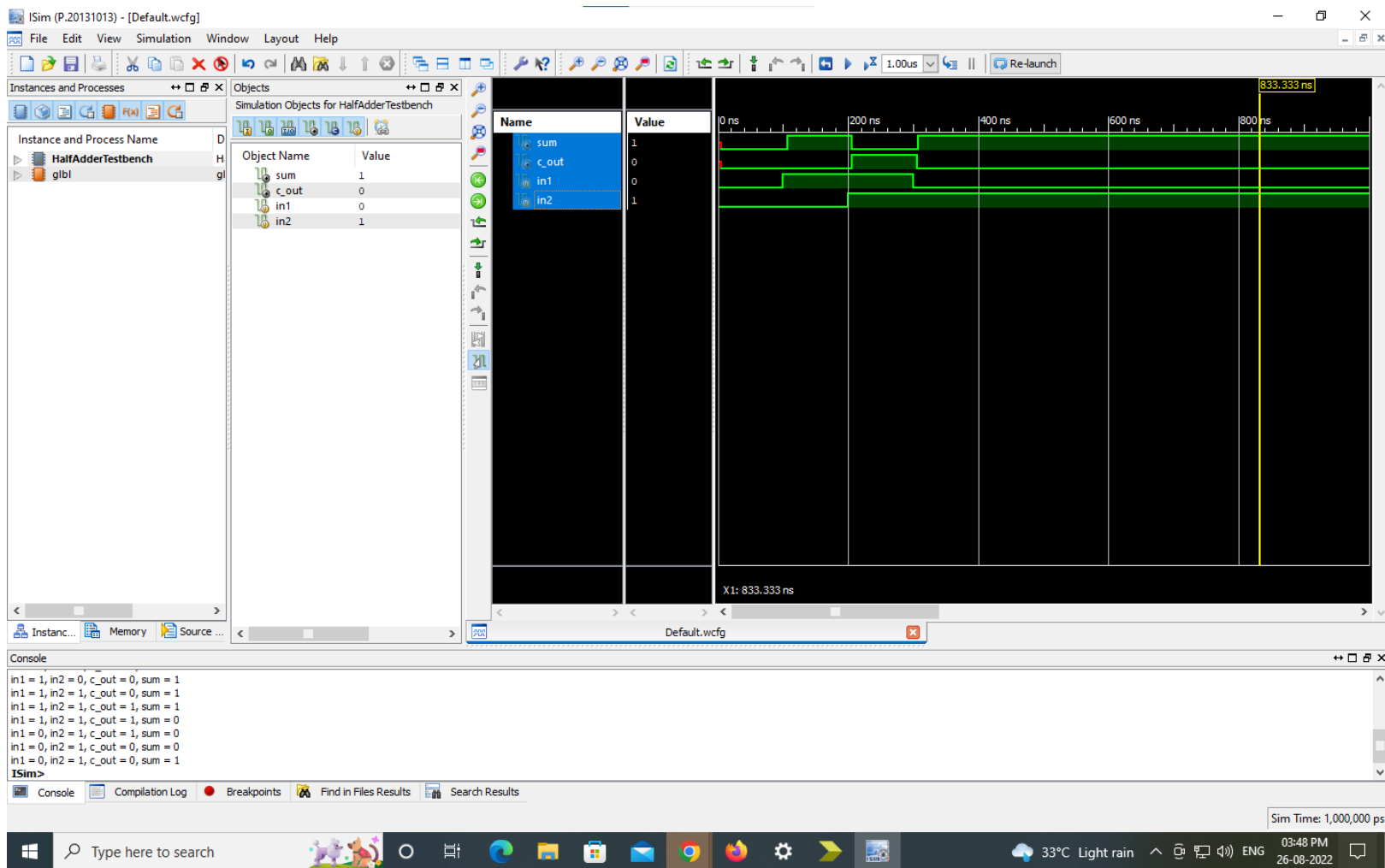


Full adder

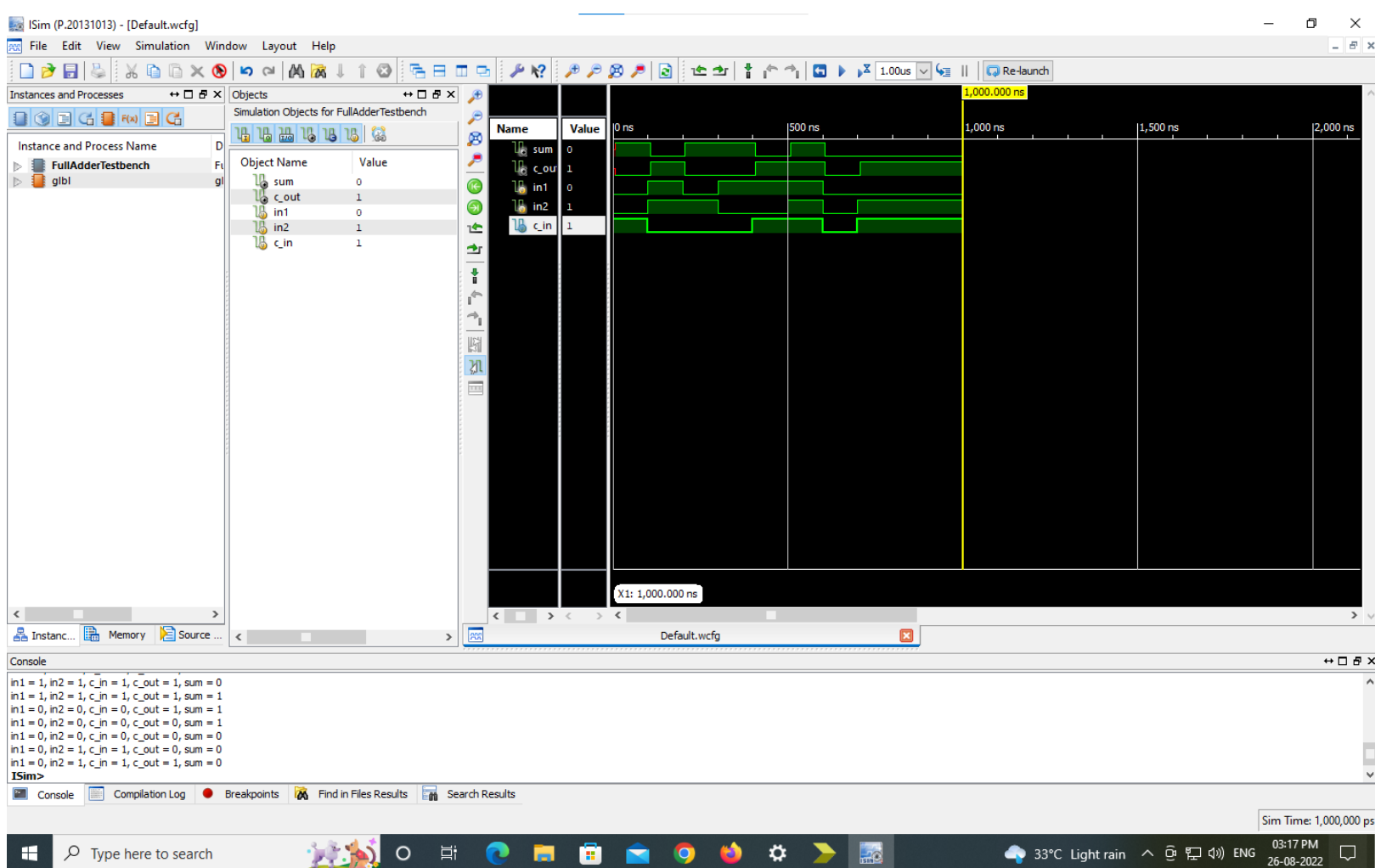


8 – bit RCA

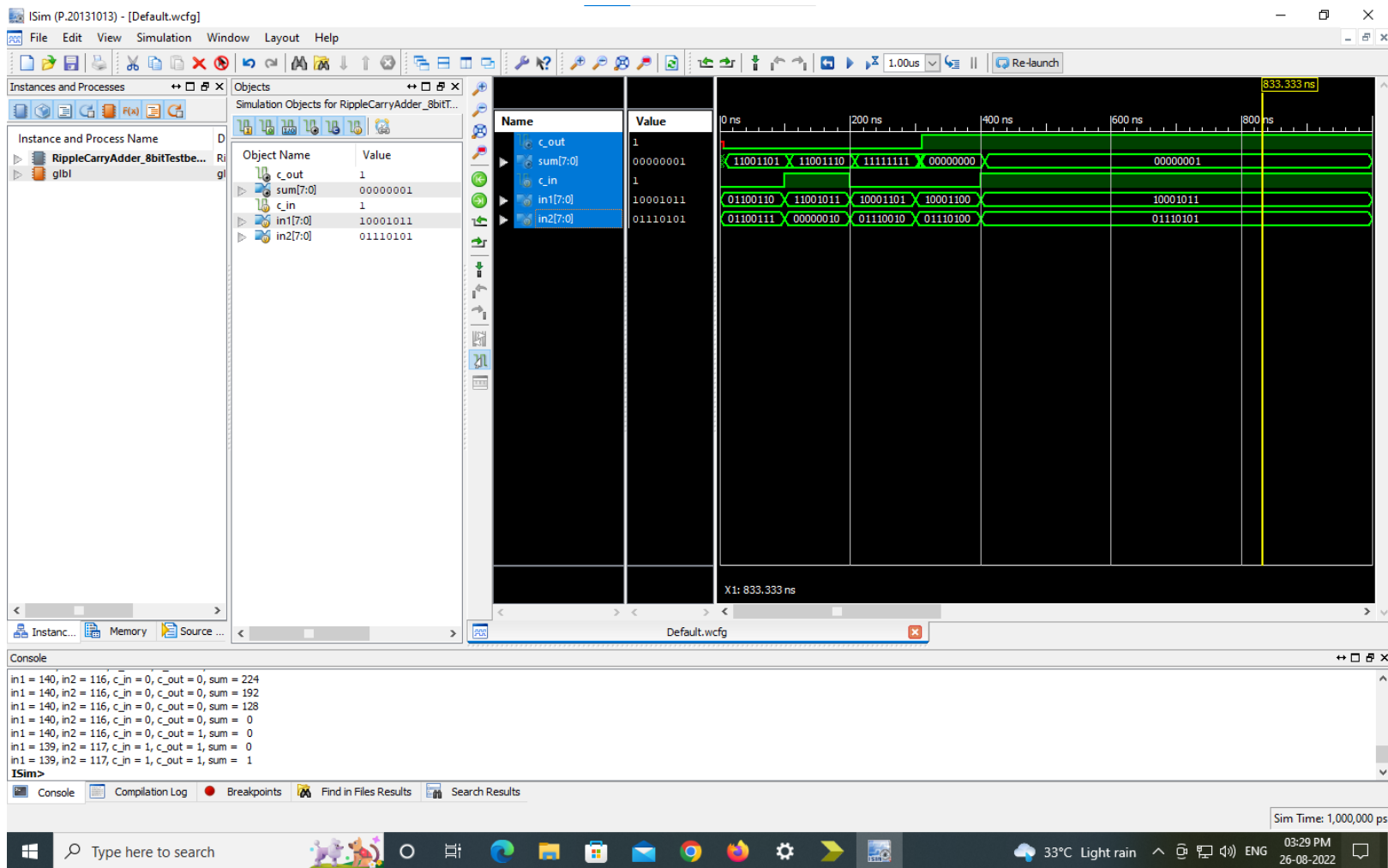


16 – bit RCA

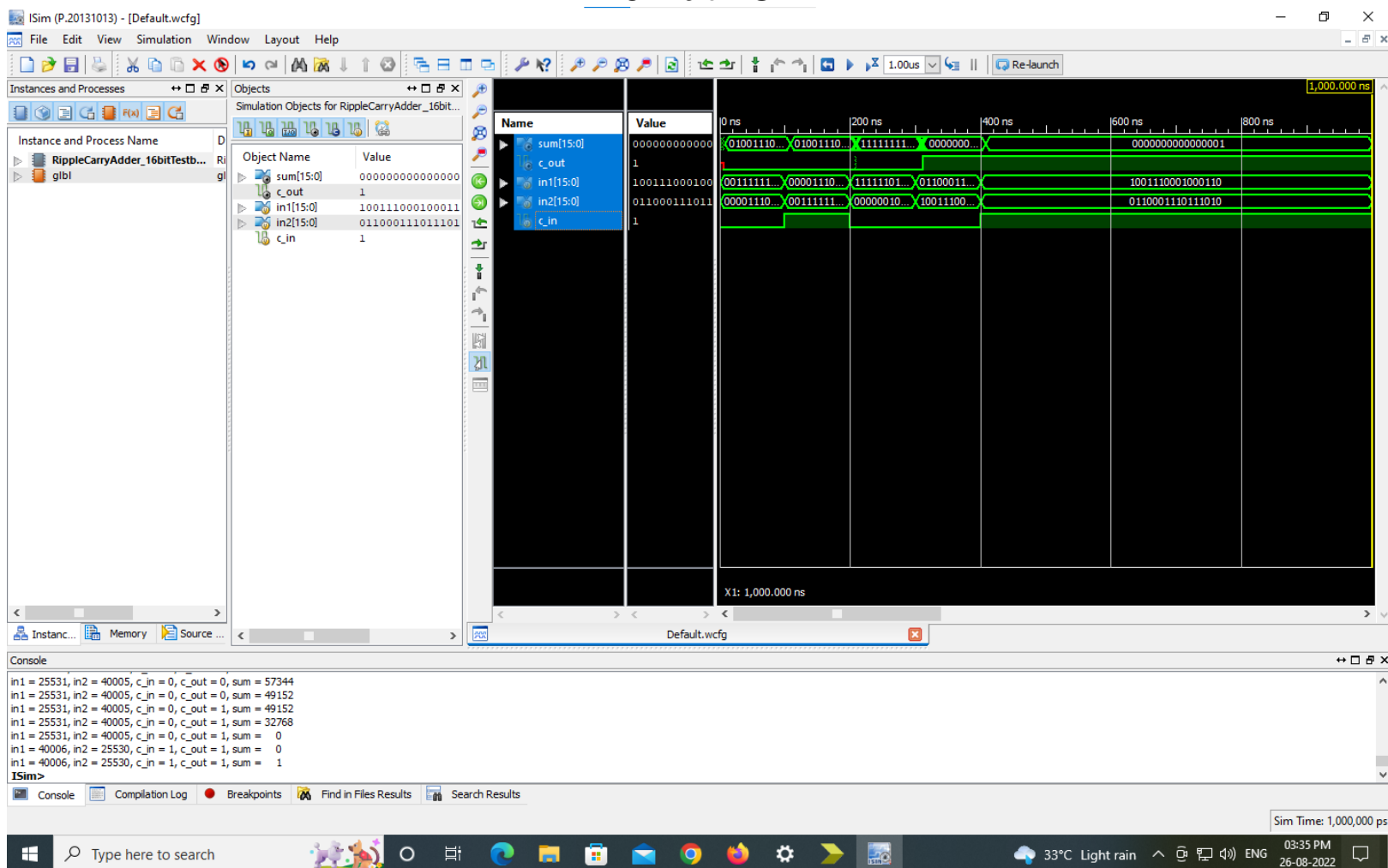

32 – bit RCA

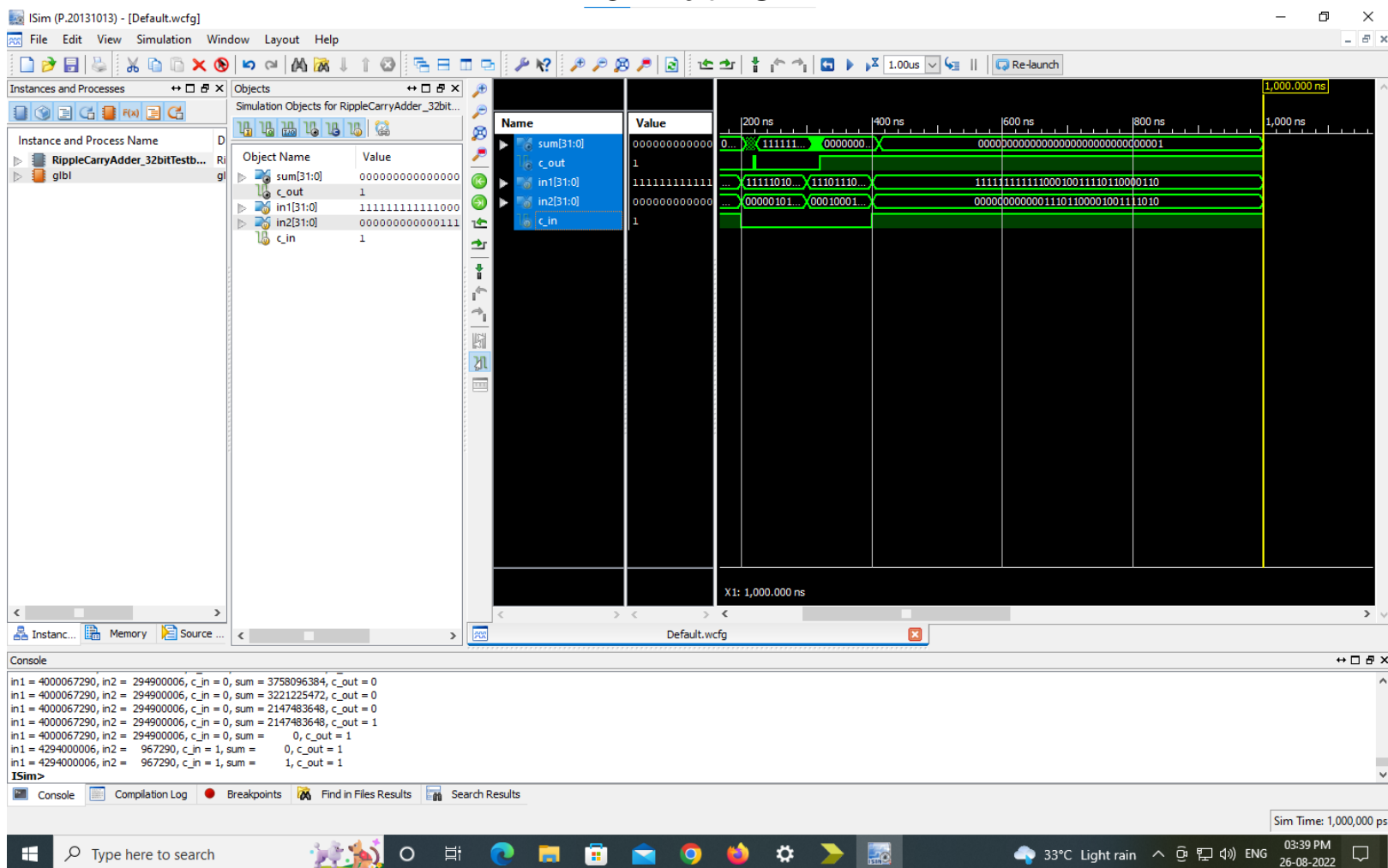

64 – bit RCA

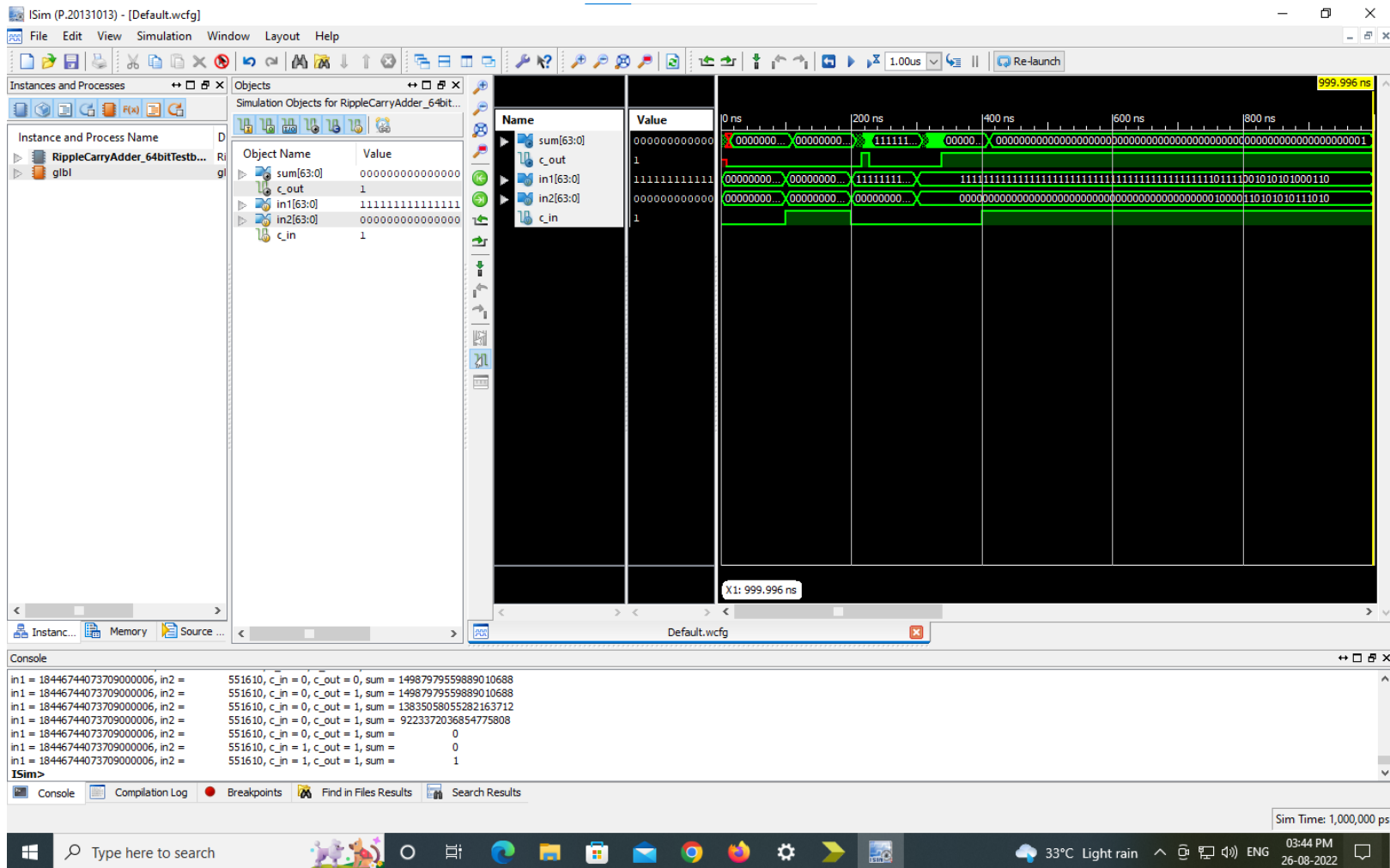

Q. How can you use the above circuit, to compute the difference between two n-bit numbers?

Ans: $(a - b)$ can be written as $(a + (-b))$. We observe that $(-b)$ is the 2's complement of b . So, $(-b)$ can be written as $(\sim b + 1)$. Now, $\sim b$ is 1's complement of b . so $(a - b)$ is RCA(a , $\sim b$, 1) where 1 is the carry in and a and $\sim b$ are the two inputs.

In the circuit, we can connect a switch to the carry in of the adder, as well as XOR gates to each of b 's input bits. When the switch is turned on, the carry in bit becomes 1 and all the bits of b are simultaneously flipped (XOR with 1 flips the bit value). In this manner, we shall obtain $a - b$ as output. When the switch is turned off, nothing changes and we obtain $a + b$ in output.

Post Route of Difference between two 64 bit numbers

